 


To make program run:

- 1) Open .qar file.
- 2) Compile project.
- 3) Open modelsim and compile all the files in the restored folder.
- 4) simulate MiniMips\_w\_instruction\_tb.v file.
- 5) Press run button again until the program ends.

Instr	E3 E2 E1 E0 Opcode	F2 F1 F0 Func	P2 P1 P0 ALUOp	Desired ALU action	C2 C1 C0 ALUctr	RegDst	ALUSrc	Memto Reg	Reg Wrt	Mem Read	Mem Write	Branch
AND	0000	000	000	AND	110	1	0	0	1	0	0	0
ADD	0000	001	000	ADD	000	1	0	0	1	0	0	0
SUB	0000	010	000	SUB	010	1	0	0	1	0	0	0
XOR	0000	011	000	XOR	001	1	0	0	1	0	0	0
NOR	0000	100	000	NOR	101	1	0	0	1	0	0	0
OR	0000	101	000	OR	111	1	0	0	1	0	0	0
ADDI	0001	XXX	001	ADD	000	0	1	0	1	0	0	0
ANDI	0010	XXX	010	AND	110	0	1	0	1	0	0	0
ORI	0011	XXX	011	OR	111	0	1	0	1	0	0	0
NORI	0100	XXX	100	NOR	101	0	1	0	1	0	0	0
BEQ	0101	XXX	101	SUB	010	x	0	x	0	0	0	1
BNE	0110	XXX	101	SUB	010	x	0	x	0	0	0	1
SLTI	0111	XXX	110	SLT	100	0	1	0	1	0	0	0
LW	1000	XXX	111	ADD	000	0	1	1	1	1	0	0
SW	1001	XXX	111	ADD	000	x	1	X	0	0	1	0



$$\text{Func} + \text{ALUop} \Rightarrow \text{ALUctr}$$

$$C2 = (\bar{P2} \bar{P1} \bar{P0}) (F2 + \bar{F1} \bar{F0}) + (\bar{P2} P1 + P2 \bar{P0})$$

$$C1 = (\bar{P2} \bar{P1} \bar{P0}) (F2 \odot F0) + (\bar{P2} P1 + P2 \bar{P1} P0)$$

$\downarrow$   
 XOR

$$C0 = (\bar{P2} \bar{P1} \bar{P0}) (F2 + F1 F0) + (\bar{P2} \bar{P1} \bar{P0} + \bar{P2} P1 P0)$$

$$P2 = E3 + E2$$

$$P1 = E3 + E1 E0 + \bar{E2} E1 = E3 + E1 (E0 + \bar{E2})$$

$$\begin{aligned}
 P0 &= E3 + \bar{E1} E0 + \bar{E2} E1 E0 + E2 E1 \bar{E0} \\
 &= E3 + \bar{E1} E0 + E1 (\underbrace{\bar{E2} E0 + E2 \bar{E0}}_{\text{XOR}}) \\
 &= E3 + \bar{E1} E0 + E1 (E2 \oplus E0)
 \end{aligned}$$

$$R = \overline{E3} \overline{E2} \overline{E1} \overline{E0}$$

$$I = \overline{R} (\overline{P2} \overline{P0})$$

$$B = E2 (E1 \oplus E0) \Rightarrow 101 + 110$$

$$LW = \overline{E3} \overline{E0}$$

$$SW = E3 E0$$

$$RegDst = R$$

$$ALUSrc = I + LW + SW$$

$$MemtoReg = LW$$

$$RegWrt = R + I + LW$$

$$MemRead = LW$$

$$MemWrite = SW$$

$$Branch = B$$

Main control testbench:

```

initial begin
  opCode[3:0] = 4'b0000;
  func[2:0] = 3'b000;
  #`DELAY;
  opCode[3:0] = 4'b0000;
  func[2:0] = 3'b001;
  #`DELAY;
  opCode[3:0] = 4'b0000;
  func[2:0] = 3'b010;
  #`DELAY;
  opCode[3:0] = 4'b0000;
  func[2:0] = 3'b011;
  #`DELAY;
  opCode[3:0] = 4'b0000;
  func[2:0] = 3'b100;
  #`DELAY;
  opCode[3:0] = 4'b0000;
  func[2:0] = 3'b101;
  #`DELAY;

  opCode[3:0] = 4'b0001;
  #`DELAY;
  opCode[3:0] = 4'b0010;
  #`DELAY;
  opCode[3:0] = 4'b0011;
  #`DELAY;
  opCode[3:0] = 4'b0100;
  #`DELAY;
  opCode[3:0] = 4'b0101; |
  #`DELAY;
  opCode[3:0] = 4'b0110;
  #`DELAY;
  opCode[3:0] = 4'b0111;
  #`DELAY;
  opCode[3:0] = 4'b1000;
  #`DELAY;
  opCode[3:0] = 4'b1001;
  #`DELAY;

VSI647> run
# time = 0, a=0, b=0 , aluCtrl= 110,RegDst= 1,ALUSrc= 0,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 0
# time = 10, a=0, b=1 , aluCtrl= 0,RegDst= 1,ALUSrc= 0,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 0
# time = 20, a=0, b=10 , aluCtrl= 10,RegDst= 1,ALUSrc= 0,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 0
# time = 30, a=0, b=11 , aluCtrl= 1,RegDst= 1,ALUSrc= 0,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 0
# time = 40, a=0, b=100 , aluCtrl= 101,RegDst= 1,ALUSrc= 0,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 0
# time = 50, a=0, b=101 , aluCtrl= 111,RegDst= 1,ALUSrc= 0,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 0
# time = 60, a=1, b=101 , aluCtrl= 0,RegDst= 0,ALUSrc= 1,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 1
# time = 70, a=10, b=101 , aluCtrl= 110,RegDst= 0,ALUSrc= 1,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 1
# time = 80, a=11, b=101 , aluCtrl= 111,RegDst= 0,ALUSrc= 1,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 1
# time = 90, a=100, b=101 , aluCtrl= 101,RegDst= 0,ALUSrc= 1,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 1
VSI648> run
# time = 100, a=101, b=101 , aluCtrl= 10,RegDst= 0,ALUSrc= 0,MemtoReg= 0,RegWrt= 0,MemRead= 0,MemWrite= 0,Branch= 1,I TYPE : 0
# time = 110, a=110, b=101 , aluCtrl= 10,RegDst= 0,ALUSrc= 0,MemtoReg= 0,RegWrt= 0,MemRead= 0,MemWrite= 0,Branch= 1,I TYPE : 0
# time = 120, a=111, b=101 , aluCtrl= 100,RegDst= 0,ALUSrc= 1,MemtoReg= 0,RegWrt= 1,MemRead= 0,MemWrite= 0,Branch= 0,I TYPE : 1
# time = 130, a=1000, b=101 , aluCtrl= 0,RegDst= 0,ALUSrc= 1,MemtoReg= 1,RegWrt= 1,MemRead= 1,MemWrite= 0,Branch= 0,I TYPE : 0
# time = 140, a=1001, b=101 , aluCtrl= 0,RegDst= 0,ALUSrc= 1,MemtoReg= 0,RegWrt= 0,MemRead= 0,MemWrite= 1,Branch= 0,I TYPE : 0

VSI648>

```

Mux2x1ThreeBit test:

```

mux2x1ThreeBits mux(write_reg,read_reg2,write_regRegDst1,RegDst);

initial begin
  read_reg2[2:0] = 3'b110; write_regRegDst1[2:0] = 3'b001; RegDst = 1'b0;
  #`DELAY;
  read_reg2[2:0] = 3'b100; write_regRegDst1[2:0] = 3'b011;RegDst = 1'b1;
  #`DELAY;
  read_reg2[2:0] = 3'b110; write_regRegDst1[2:0] = 3'b111;RegDst = 1'b0;
  #`DELAY;
  read_reg2[2:0] = 3'b010; write_regRegDst1[2:0] = 3'b101;RegDst = 1'b1;
end

```

```

# time = 0, read_reg2 =110, b=1, sum=110,regdst = 0
# time = a, read_reg2 =100, b=11, sum=11,regdst = 1
# time = 14, read_reg2 =110, b=111, sum=110,regdst = 0
# time = 1e, read_reg2 =10, b=101, sum=101,regdst = 1

```

VSIM 651>

Instruction Memory test:

```

1  `define DELAY 10
2  module instruction_memory_tb();|
3  reg clk;
4  wire [15:0] instruction_set;
5  wire [31:0] newPc;
6
7  reg [31:0] readAddress;
8  instruction_memory uut(instruction_set,newPc,readAddress,clk);
9  initial
10 begin
11     clk = 1'b1;
12     readAddress <=0;
13 end
14 always
15 begin
16     #1 clk = ~clk;
17 end
18 always
19 begin
20     #`DELAY;
21     if(readAddress>29)
22     begin
23         $stop;
24     end
25     else
26     begin
27         readAddress<=newPc;
28     end
29 end
30 initial begin
31     $readmemb("instructions.txt", uut.instructions);
32 end
33
34 initial
35 begin
36     $monitor("time : %1d,instruction: %1b, address = %1d,newPc=%1d", $time,instruction_set,readAddress,newPc);
37 end
38 endmodule

```

```

VSIM 706> run
# time : 0,instruction: x, address = 0,newPc=x
# time : 2,instruction: 1010011000, address = 0,newPc=1
# time : 10,instruction: 1010011000, address = 1,newPc=1
# time : 12,instruction: 1001001011000110, address = 1,newPc=2
# time : 20,instruction: 1001001011000110, address = 2,newPc=2
# time : 22,instruction: 1000001101000110, address = 2,newPc=3
# time : 30,instruction: 1000001101000110, address = 3,newPc=3
# time : 32,instruction: 101011101000001, address = 3,newPc=4
# time : 40,instruction: 101011101000001, address = 4,newPc=4
# time : 42,instruction: 1101111010001, address = 4,newPc=5
# time : 50,instruction: 1101111010001, address = 5,newPc=5
# time : 52,instruction: 1101001010001, address = 5,newPc=6
# time : 60,instruction: 1101001010001, address = 6,newPc=6
# time : 62,instruction: 110011100000001, address = 6,newPc=7
# time : 70,instruction: 110011100000001, address = 7,newPc=7
# time : 72,instruction: 1101001011101, address = 7,newPc=8
# time : 80,instruction: 1101001011101, address = 8,newPc=8
# time : 82,instruction: 110011101000001, address = 8,newPc=9
# time : 90,instruction: 110011101000001, address = 9,newPc=9
# time : 92,instruction: 1101110000001, address = 9,newPc=10
VSIM 707> run
# time : 100,instruction: 1101110000001, address = 10,newPc=10
# time : 102,instruction: 110010100000, address = 10,newPc=11
# time : 110,instruction: 110010100000, address = 11,newPc=11
# time : 112,instruction: 100010011001, address = 11,newPc=12
# Break in Module instruction_memory_tb at D:/ORG_HW4/DraftForHW4_restored/instruction_memory_tb.v line 23

```

## Branch unit test:

```

initial begin
  beqCommand = 1'b1;
  noBranchNewPc = 32'hFB;
  write_data = 32'h0;
  imm = 32'h4;
  Branch = 1'b1;
  #`DELAY; // branch == successful

  beqCommand = 1'b1;
  noBranchNewPc = 32'hFB;
  write_data = 32'h0;
  imm = 32'h4;
  Branch = 1'b0;
  #`DELAY; // branch != successful

  beqCommand = 1'b1;
  noBranchNewPc = 32'hFB;
  write_data = 32'hF;
  imm = 32'h4;
  Branch = 1'b1;
  #`DELAY; // branch != successful

  beqCommand = 1'b0;
  noBranchNewPc = 32'hFB;
  write_data = 32'hF;
  imm = 32'h4;
  Branch = 1'b1;
  #`DELAY; // branch == successful

  beqCommand = 1'b0;
  noBranchNewPc = 32'hFB;
  write_data = 32'h0;
  imm = 32'h4;
  Branch = 1'b1;
  #`DELAY; // branch != successful

  beqCommand = 1'b0;
  noBranchNewPc = 32'hFB;
  write_data = 32'hF;
  imm = 32'h4;
  Branch = 1'b0;
  #`DELAY; // branch != successful
end

```

```

# time = 0, beqCommand = 1, noBranchNewPc=fb, write_data=0,imm=4,Branch=1, newPc = ff
# time = a, beqCommand = 1, noBranchNewPc=fb, write_data=0,imm=4,Branch=0, newPc = fb
# time = 14, beqCommand = 1, noBranchNewPc=fb, write_data=f,imm=4,Branch=1, newPc = fb
# time = 1e, beqCommand = 0, noBranchNewPc=fb, write_data=f,imm=4,Branch=1, newPc = ff
# time = 28, beqCommand = 0, noBranchNewPc=fb, write_data=0,imm=4,Branch=1, newPc = fb
# time = 32, beqCommand = 0, noBranchNewPc=fb, write_data=f,imm=4,Branch=0, newPc = fb

```

## Data memory test:

```

data_memory dm(read_data,write_data, address, mem_write, mem_read,clk );
initial
begin
    clk = 1'b1;
end
always
begin
    #1 clk = ~clk;
end
initial
begin
    write_data = 32'hFF;
    address = 32'h5;
    mem_write = 1'b1;
    mem_read = 1'b0;
    #`DELAY;

    address = 32'h5;
    mem_write = 1'b0;
    mem_read = 1'b1;
    #`DELAY;

    write_data = 32'hFFFF_ABCD;
    address = 32'h5;
    mem_write = 1'b1;
    mem_read = 1'b0;
    #`DELAY;

    address = 32'h5;
    mem_write = 1'b0;
    mem_read = 1'b1;
    #`DELAY;

end
initial begin
$readmemb("data.txt", dm.memory);
end
initial
begin
$monitor("time : %1d,writeCommand: %1b, address = %1h,written=%1h, readCommand = %1b,read: %1h",$time,mem_write,address,write_data,mem_read,read_data);

```

```

# time : 0,writeCommand: 1, address = 5,written=ff, readCommand = 0,read: x
# time : 10,writeCommand: 0, address = 5,written=ff, readCommand = 1,read: ff
# time : 20,writeCommand: 1, address = 5,written=ffffabcd, readCommand = 0,read: ff
# time : 30,writeCommand: 0, address = 5,written=ffffabcd, readCommand = 1,read: ffffabcd

```

## ExtendImm test:

```

1  `define DELAY 10
2  module extendImm_tb();
3  reg[5:0] imm;
4  wire [31:0] extended;
5
6  extendImm extend(extended,imm);
7
8
9  initial begin
10     imm[5:0] = 6'hF;
11     #`DELAY;
12     imm[5:0] = 6'b111111;
13     #`DELAY;
14     imm[5:0] = 6'b001011;
15     #`DELAY;
16     end
17
18
19     initial
20     begin
21         $monitor("time = %1h, imm =%1b extend=> extended=%1b ", $time, imm, extended);
22     end
23     endmodule
24

```

```

VSIM 50> run
# time = 0, imm =1111 extend=> extended=1111
# time = a, imm =111111 extend=> extended=111111
# time = 14, imm =1011 extend=> extended=1011

```

### Mips registers test:

```

9 mips_registers mr( read_data_1, read_data_2, write_data, read_reg_1, read_reg_2, write_reg, signal_reg_write, clk );
10 initial
11   begin
12     clk = 1'b1;
13   end
14
15 always
16   begin
17     #1 clk = ~clk;
18   end
19 initial
20   begin
21     write_data = 32'hFFFF_AAAA;
22     write_reg = 3'h1;
23     signal_reg_write = 1'b1;
24     #`DELAY;
25
26     read_reg_1 = 3'h1;
27     signal_reg_write = 1'b0;
28     #`DELAY;
29
30     write_data = 32'hFFFF_AAAA; // Zero register's content can not be changed
31     write_reg = 3'h0;
32     signal_reg_write = 1'b1;
33     #`DELAY;
34
35     read_reg_1 = 3'h0;
36     signal_reg_write = 1'b0;
37     #`DELAY;
38   end
39 initial begin
40   $readmemb("registers.mem", mr.registers);
41
42   .....
43   # time : 0,read_data_1 = x, read_data_2= x, write_data= ffffffff, read_reg_1= x, read_reg_2= x, write_reg= 1, signal_reg_write= 1
44   # time : 10,read_data_1 = ffffffff, read_data_2= x, write_data= ffffffff, read_reg_1= 1, read_reg_2= x, write_reg= 1, signal_reg_write= 0
45   # time : 20,read_data_1 = ffffffff, read_data_2= x, write_data= ffffffff, read_reg_1= 1, read_reg_2= x, write_reg= 0, signal_reg_write= 1
46   # time : 30,read_data_1 = 0, read_data_2= x, write_data= ffffffff, read_reg_1= 0, read_reg_2= x, write_reg= 0, signal_reg_write= 0
47

```

### Mux2x1 32 Bit test:

```

`define DELAY 10
module mux2x1_32Bits_tb();

reg[31:0] input1,input2;
wire[31:0] out;
reg select;

mux2x1_32Bits mux(out,input1,input2,select);
initial begin
input1 = 32'b110; input2 = 32'b001; select = 1'b0;
#`DELAY;
input1 = 32'b110; input2 = 32'b001; select = 1'b1;
#`DELAY;

end

initial
begin
$monitor("time = %1h, input1 = %1b,input2 = %1b,select = %1b,output = %1b", $time, input1,input2,select,out);
end
endmodule

.....
# time = 0, input1 = 110,input2 = 1,select = 0,output = 110
# time = a, input1 = 110,input2 = 1,select = 1,output = 1

```



MiniMips test:

```
MiniMips_w_instruction uut(pc,clk,instruction_set, newPc);
initial
begin
    clk = 1'b0;
    pc <= 0;
end
always
begin
    #1 clk = ~clk;
end
always
begin
    #`DELAY;
    if(pc>35)
    begin
        $writememb("registers_outp.mem", uut.mipsregisters.registers);
        $writememb("data_memory_outp.mem", uut.DataMemory.memory);
        $stop;
    end
    else
    begin
        pc<=newPc;
        $writememb("registers_outp.mem", uut.mipsregisters.registers);
        $writememb("data_memory_outp.mem", uut.DataMemory.memory);
        // to be able to see result of instructions one by one, stop command must be activated
        //$stop;
    end
end
initial begin
    $readmemb("registers.mem", uut.mipsregisters.registers);
    $readmemb("data.txt", uut.DataMemory.memory);
    $readmemb("instructions.txt", uut.instructionMemory.instructions);
end
```

I do not know if the usage of 'if' to make program end is forbidden, but I could not find any other way to do it.

Instructions:

```
instructions.txt X
D: > ORG_HW4 > DraftForHW4_restored > s
1 0000001010011000
2 1001001011000110
3 1000001101000110
4 0101011101000001
5 0001_101_111_010001
6 0001101001010001
7 0110011100000001
8 0001_101_001_011101
9 0110011101000001
10 0001_101_110_000001
11 0000_110_010_100_000
12 0000_100_010_011_001
13 0000_100_011_001_001
14 0000_101_100_010_010
15 0000_111_100_011_010
16 0000_111_011_010_011
17 0000_111_001_110_011
18 0000_111_011_100_100
19 0000_111_001_101_100
20 0000_001_110_010_101
21 0000_001_011_111_101
22 0010_101_001_111111
23 0010_001_011_110111
24 0011_101_001_111000
25 0011_001_011_101010
26 0100_101_001_111000
27 0100_001_011_100010
28 0111_001_100_111000
29 0111_100_101_100010
30 1001_101_111_000111
31 1000_101_001_000111
32 0011_011_001_111111
33 0011_011_000_111111
```

Registers at start:

```
registers.mem X data.txt instructionsWithExplanation.txt
D: > ORG_HW4 > DraftForHW4_restored > simulation > modelsim > registers.mem
1 00000000000000000000000000000000
2 00000000000000000000000000001010
3 000000000000000000000000000010010
4 00000000000000000000000000000011
5 00000000000000000000000000000100
6 0000000000000000000000000000100101
7 00000000000000000110000001111101
8 00000000000000000000000001000111
```

Memory at the start:

```
Explorer (Ctrl+Shift+E)  data.txt  X  instruct
D: > ORG_HW4 > DraftForHW4_restored > simulation >

1  00000000000000000000000000000000
2  00000000000000000000000000000001
3  00000000000000000000000000000010
4  00000000000000000000000000000011
5  00000000000000000000000000000100
6  00000000000000000000000000000101
7  00000000000000000000000000000110
8  00000000000000000000000000000111
9  00000000000000000000000000001000
10 00000000000000000000000000001001
11 00000000000000000000000000001010
12 00000000000000000000000000001011
13 00000000000000000000000000001100
14 00000000000000000000000000001101
15 00000000000000000000000000001110
16 00000000000000000000000000001111
17 00000000000000000000000000001000
```

Registers at the end:

```
registers_outp.mem  X  data_memory_outp.mem  dat
G_HW4 > DraftForHW4_restored > simulation > modelsim > registers_
1  // memory data file (do not edit the following
2  // instance=/MiniMips_w_instruction_tb/uut/mips
3  // format=bin addressradix=h dataradix=b versio
4  00000000000000000000000000000000
5  11111111111111111111111110111111
6  00000000000000000000000000001010111
7  11111111111111111111111110011000
8  000000000000000000000000000000000
9  000000000000000000000000000000001
10 00000000000000000000000000001010001
11 00000000000000000000000000001010111
12
```

Data Memory at the end:

```

≡ registers_outp.mem  ≡ data_memory_outp.mem >
RG_HW4 > DraftForHW4_restored > simulation > modelsim >
1 // memory data file (do not edit the fo
2 // instance=/MiniMips_w_instruction_tb/
3 // format=bin addressradix=h dataradix=
4 00000000000000000000000000000000
5 00000000000000000000000000000001
6 00000000000000000000000000000010
7 00000000000000000000000000000011
8 00000000000000000000000000000100
9 00000000000000000000000000000101
10 00000000000000000000000000000110
11 00000000000000000000000000000001
12 00000000000000000000000001010111
13 0000000000000000000000000001001
14 0000000000000000000000000001010
15 0000000000000000000000000001011
16 0000000000000000000000000001100
17 0000000000000000000000000001101
18 0000000000000000000000000001110
19 0000000000000000000000000001111
20 000000000000000000000000000010
21 00000000000000000000000000010001
22 00000000000000000000000000010010

```

Instructions and their explanation, I also added this part as txt file, whose name is instructionsWithExplanation.txt:

0000001010011000 R3 = R1 & R2, R1 = 1010, R2 = 10010, R3 will become 10

1001001011000110 sw R3,R1(6), Mem[16] = 32'b10

1000001101000110 lw R5,R1(6), R5 = 32'b10

0101011101000001 // beq r3,r5,1, next command will not work

0001101111010001 addi R7,R5,10001(in binary) r7 will become 10 + 10001 = 10011

0101011100000001 // beq r3,r4,1, next command will work r3!=r4

0001101001010001 addi R1,R5,10001(in binary) r1 will become 10 + 10001 = 10011

0110011100000001 //bneq r3, r4,1 next command will not work r3!=r4

0001\_101\_001\_011101 addi R1,R5,11101(in binary) r1 will not become 10 + 11101 = 11111, it will stay same

0110011101000001 //bneq r3, r5,1 next command will work r3==r5

0001\_101\_110\_000001 addi R6,R5,11101(in binary) r6 will become 10 + 000001 = 11,

/\*

registers:

0: 00000000000000000000000000000000  
1: 0000000000000000000000000000010011  
2: 0000000000000000000000000000010010  
3: 0000000000000000000000000000000010  
4: 00000000000000000000000000000000100  
5: 00000000000000000000000000000000010  
6: 00000000000000000000000000000000011  
7: 00000000000000000000000001000111

\*/

0000\_110\_010\_100\_000 R4 = R6 & R2, R6 = 11, R2 = 10010, R4 will become 10

0000\_100\_010\_011\_001 R3 = r4 + r2, r4 = 10, r2 = 10010, r3 will become 10100

0000\_100\_011\_001\_001 R1 = r4 + r3, r4 = 10, r3 = 10100, r1 will become 10110

/\*

registers:

0: 00000000000000000000000000000000  
1: 0000000000000000000000000000010110  
2: 0000000000000000000000000000010010  
3: 0000000000000000000000000000010100  
4: 00000000000000000000000000000000010  
5: 00000000000000000000000000000000010  
6: 00000000000000000000000000000000011  
7: 00000000000000000000000001000111

\*/

sub:

0000\_101\_100\_010\_010 => R2 = R5 - R4, R2 will become 0

0000\_111\_100\_011\_010 => R3 = R7 - R4, R3 will become 1000111 - 10 = 1000101

/\*

registers:

00000000000000000000000000000000

0000000000000000000000000000010110

R2: 00000000000000000000000000000000

R3: 00000000000000000000000000001000101

R4: 0000000000000000000000000000000010

R5: 0000000000000000000000000000000010

0000000000000000000000000000000011

R7: 00000000000000000000000000001000111

\*/

xor:

0000\_111\_011\_010\_011 // r2 = r7 xor r3 => r2 will be 10

0000\_111\_001\_110\_011 // r6 = r7 xor r1 => r6 will be 1010001

/\*

registers:

00000000000000000000000000000000

0000000000000000000000000000010110

R2: 0000000000000000000000000000000010

00000000000000000000000000001000101

0000000000000000000000000000000010

0000000000000000000000000000000010

R6: 00000000000000000000000000001010001

00000000000000000000000000001000111

\*/

//nor



0010\_101\_001\_111111 andi R1,R5,111111(in binary) r1 will become 101000

0010\_001\_011\_110111 andi R3,R1,110111(in binary) r3 will become 100000

/\*

registers:

00000000000000000000000000000000

r1: 0000000000000000000000000101000

00000000000000000000000001010111

r3: 0000000000000000000000000100000

11111111111111111111111110111000

11111111111111111111111110101000

00000000000000000000000001010001

00000000000000000000000001010111

\*/

0011\_101\_001\_111000 ori R1,R5,111000(in binary) r1 will become

11111111111111111111111110111000

0011\_001\_011\_101010 ori R3,R1,101010(in binary) r3 will become

11111111111111111111111110111010

/\*

registers:

00000000000000000000000000000000

r1: 11111111111111111111111110111000

00000000000000000000000001010111

r3: 11111111111111111111111110111010

11111111111111111111111110111000

11111111111111111111111110101000

00000000000000000000000001010001

00000000000000000000000001010111

\*/

0100\_101\_001\_111000 nori R1,R5(11111111111111111111111110101000),111000(in binary) r1 will become 1000111

0100\_001\_011\_100010 nori R3,R1(1000111),100010(in binary) r3 will become

11111111111111111111111110011000



/\*

registers:

00000000000000000000000000000000  
00000000000000000000000000001000111  
00000000000000000000000000001010111  
11111111111111111111111111110011000  
11111111111111111111111111110111000  
11111111111111111111111111110101000  
00000000000000000000000000001010001  
00000000000000000000000000001010111

\*/

0111\_001\_100\_111000 slti R4,R1(1000111),111000(in binary) r4 will become 0

0111\_100\_101\_100010 slti R5,R4(0),100010(in binary) r5 will become 1

/\*

registers:

00000000000000000000000000000000  
00000000000000000000000000001000111  
00000000000000000000000000001010111  
11111111111111111111111111110011000  
r4: 00000000000000000000000000000000  
r5: 000000000000000000000000000000001  
00000000000000000000000000001010001  
00000000000000000000000000001010111

\*/

1001\_101\_111\_000111 sw R7,R5(7), Mem[7 + 1(r5 = 5)] = Mem[8] = 1010111

```
/*
```

```
Memory:
```

```
[0] = 00000000000000000000000000000000
```

```
[1] = 00000000000000000000000000000001
```

```
[2] = 00000000000000000000000000000010
```

```
[3] = 00000000000000000000000000000011
```

```
[4] = 00000000000000000000000000000100
```

```
[5] = 00000000000000000000000000000101
```

```
[6] = 00000000000000000000000000000110
```

```
[7] = 00000000000000000000000000000001
```

```
[8] = 00000000000000000000000001010111
```

```
*/
```

```
1000_101_001_000111 lw R1,R5(7), R1 = 1010111
```

```
/*
```

```
registers:
```

```
00000000000000000000000000000000
```

```
R1: 00000000000000000000000001010111
```

```
00000000000000000000000001010111
```

```
111111111111111111111111110011000
```

```
00000000000000000000000000000000
```

```
00000000000000000000000000000001
```

```
00000000000000000000000001010001
```

```
00000000000000000000000001010111
```

```
*/
```

```
//ORI
```

```
0011_011_001_111111 // ORI R1, R3, 111111 in binary
```

```
/*
```

```
R3 = 111111111111111111111111110011000
```

```
Imm= 00000000000000000000000111111
```

**\* /**